#### **Build documentation for:**

## ROLAND 100M 121 VCF

Layouts and documentation by

# FREQUENCY CENTRAL

#### What's changed:

- CA3080 used instead of BA662A
- 2 x LF351 used instead of 4558
- 2 x back to back 22uF caps used instead of 10uF BP caps
- Addition of 12dB/Oct output
- Fixed HPF not included

#### **Colour coding:**

Red traces: +12v


Brown traces: Ground Green traces: -12v

**Grey pads:** Inputs/Outputs **Blue pads:** Expansion (see text)

Orange pads: Fit 2 x back to back (negative to negative) 22uF caps (see text)

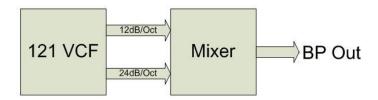
#### 12dB/Oct Output:

This output has a shallower cutoff than the 24dB/Oct output, and the frequency range is slightly offset. The 12dB/Oct output is taken from the output of the second stage. It is fed through a transistor inverting amplifier (basically a modified EH LPB1). The 12dB/Oct output is 180° out of phase with the 24dB/Oct output, therefore mixing them together results in bandpass filtering:




In practice, you'll probably be able to use two inputs of a VCA rather than having to use a dedicated mixer. The two outputs **should** be of equal volume so that 100% phase cancellation occurs, but you may need to slightly tweak the volume of one or the other, allowing for resistor tolerances.

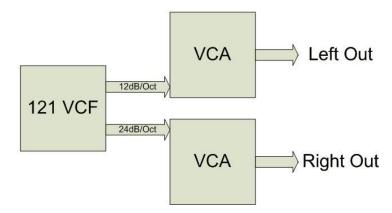Also worth feeding the two outputs to two different VCAs for stereo effects.



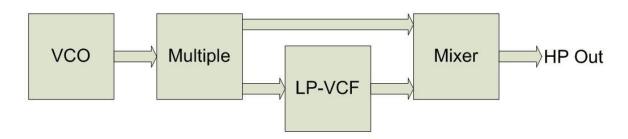...and I'm assuming you guys know how to patch a highpass filter out of a lowpass filter right? Here's how:



Then it's just a case of a little mixing, you'll find that the LP filtered signal is a little quieter than the direct signal, so set it to maximum and lower the volume of the direct signal until 100% phase cancellation occurs. In the above diagram you can use either the 12dB/Oct or the 24dB/Oct. So...... with this little filter you can do:

- 24dB/Oct lowpass
- 12dB/Oct lowpass
- 12dB/Oct bandpass
- 24dB/Oct highpass
- 12dBOct highpass


#### **Blue pads:**

- The three (3) blue pads between the Level pots allow for an additional audio input and mixing resistor.
- The three (3) blue pads between the CV pots allow for an additional CV input and mixing resistor.
- The six (6) blue pads in the lower half of the layout are 'taps' for various stage outputs. I'm convinced there's more fun to be had with this VCF, so I included extra pads for future expansion. Thinking I might run them to a mixer, with the option to


flip the phase of each, for various and weird 6dB/Oct, 18 dB/Oct, offset bandpass and highpass insanity.
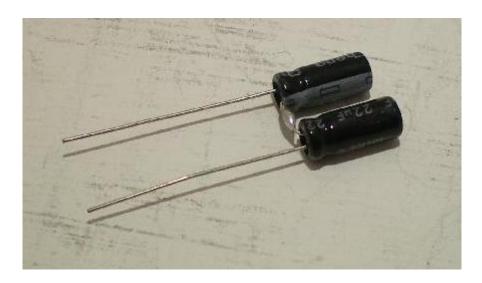
#### **Orange pads:**

The 12dB/Oct output was basically an afterthought when I realised I had a small amount of space left in the middle of the PCB after finishing the basic layout. So I added the transistor inverting amplifier. As I didn't want to start from scratch to incorporate the mod, the layout requires that you make up a bipolar cap out of two back to back (negative to negative) 22uF caps (C15 and C16) for insertion into the orange pads. Here's how:






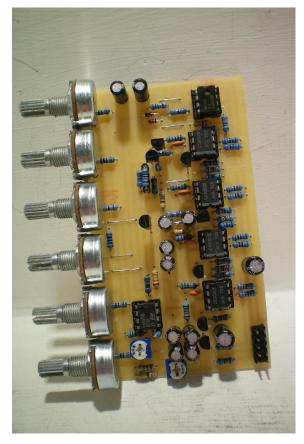


### Roland 100M 121 VCF Clone

Layout by frequencycentral

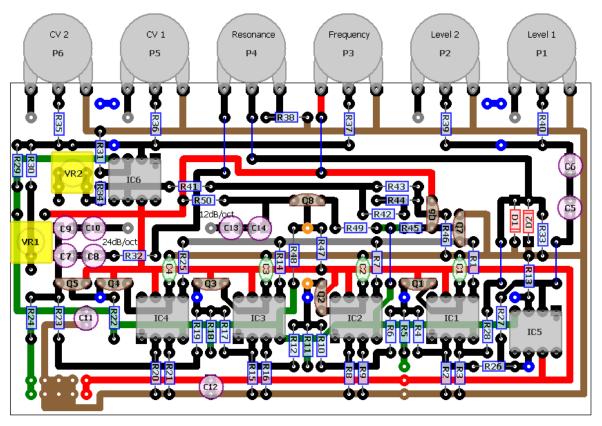

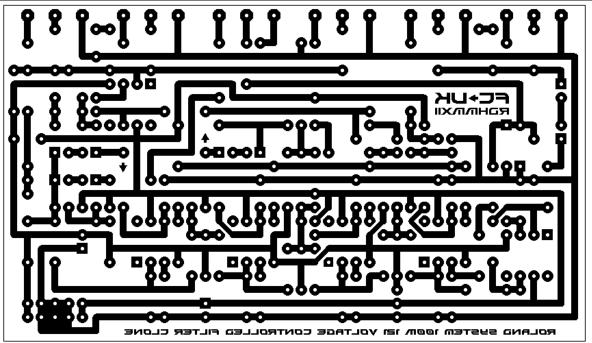Created with freeware DIY Layout Creator by Storm Software http://www.storm-software.co.yu/diy/






Resize to 48% for printing

		T	1
R1: 15K	C1: 470pF	IC1: CA3080	P1: 100k Log Alpha16mm
R2: 560R	C2: 470pF	IC2: CA3080	P2: 100k Log Alpha16mm
R3: 560R	C3: 470pF	IC3: CA3080	P3: 100k Lin Alpha16mm
R4: 68K	C4: 470pF	IC4: CA3080	P4: 100k Log Alpha16mm
R5: 22K	C5: 22uF	IC5: LF351	P5: 100k Lin Alpha16mm
R6: 68K	C6: 22uF	IC6: LF351	P6: 100k Lin Alpha16mm
R7: 15K	C7: 22uF		
R8: 560R	C8: 22uF	Q1: BF245	VR1: 100K (cutoff trim)
R9: 560R	C9: 22uF	Q2: BF245	VR2: 10K (width trim)
R10: 68K	C10: 22uF	Q3: BF245	
R11: 22K	C11: 100uF	Q4: BF245	Jumpers: Six (6)**
R12: 68K	C12: 100uF	(matched) or any DSG FET -	
R13: 33K	C13: 22uF	observe correct pinout. I ended	
R14: 15K	C14: 22uF	up using 2N5485 which are the opposite pinout. The layout	
R15: 560R	C15: 22uF (see text)	shows correct pinout for BF245.	
R16: 560R	C16: 22uF (see text)	·	
R17: 68K	, ,	Q5: BC547 NPN	
R18: 22K		Q6: BC547 NPN	
R19: 33K		Q7: BC557 PNP	
R20: 560R		Q8: BC547 NPN	
R21: 560R		Q5. B6547 W W	
R22: 22K		D1: 1n4148	
R23: 68K		D2: 1n4148	
R24: 10K		D2. 1114140	
R25: 15K			
R26: 33K			
R27: 27K			
R28: 6.8K			
R29: 270K			
R30: 1M			
R31: 10K			
R32: 10K			
R33: 10K			
R34: 15K			
R35: 100K			
R36: 100K			
R37: 150K			
R38: 100R			
R39: 100K			
R40: 100K			
R41: 10K			
R42: 1.8K			
R43: 5.6K			
R44: SDT-1000* (see below)			
· ·			
R45: 100K			
R46: 1.5K			
R47: 470K			
R48: 47K			
R49: 4.7K			
R50: 12K			

<sup>\*</sup>SDT-1000 is a 10K thermistor for temperature stability. If you're not so bothered about highly accurate 1v/oct tracking you can just use a regular 10K resistor.
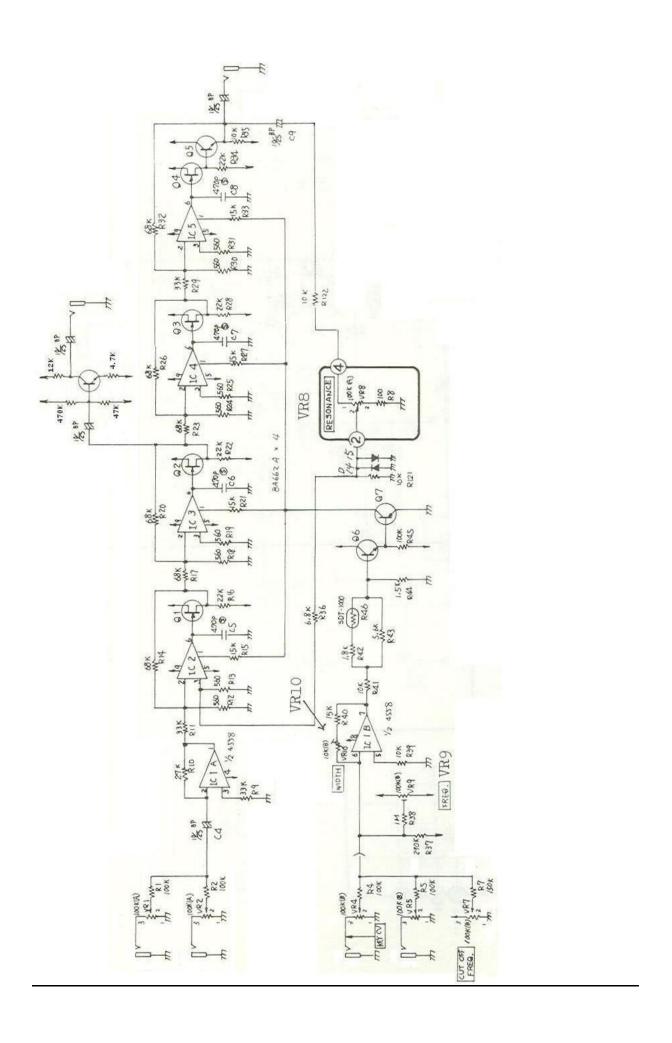
### \*\* Don't forget the six (6) jumpers!!



## PCBs available from me!

£15 GBP (including shipping) Paypal GIFT to:

rickholt22@hotmail.com

